

Department of Electrical Engineering
IIT Ropar
EE302 Analog Circuits Lab

**Experiment 2: Design and compare different
current sources.**

Keshav Kishore
2018eeb1158

Submission Date: 08/03/2021


Objectives:

- Design a current source and find its output resistance and the minimum voltage required for its operation.
- Design a cascode current source and find their output resistance and the minimum voltage required for operation.
- Design a low voltage cascode current source and find their output resistance and the minimum voltage required for operation.
- Finally, Compare all the sources

Components/Tools Required: Ltspice, Gdocs

Theory :


If we apply some input current into M1, then this current will flow through the source of M1 to ground because the gate of M2 has infinite resistance. This current will produce a suitable gate voltage (relative to ground) on M1, to satisfy the I-V square law relationship of the MOSFET. Notice then that the gate voltage of M1 is shared with the gate of M2. Therefore, M2 will have the same V_{gs} drop, and therefore the same current (if its W/L is the same).

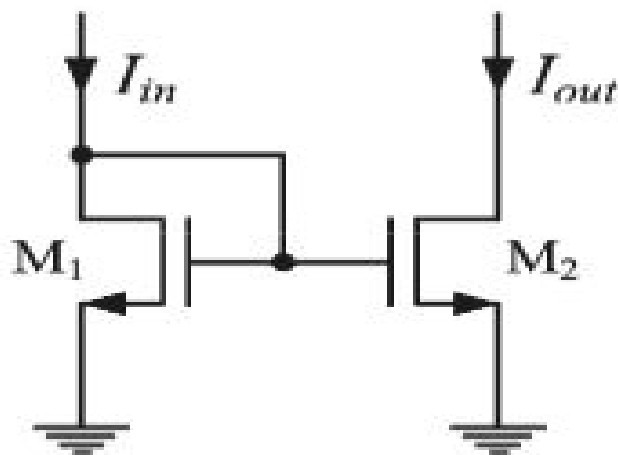


For general Case : $\frac{I_{out}}{I_{in}} = \frac{(\frac{W}{L})_{M2}}{(\frac{W}{L})_{M1}}$

Circuit Diagram:


- For basic current source

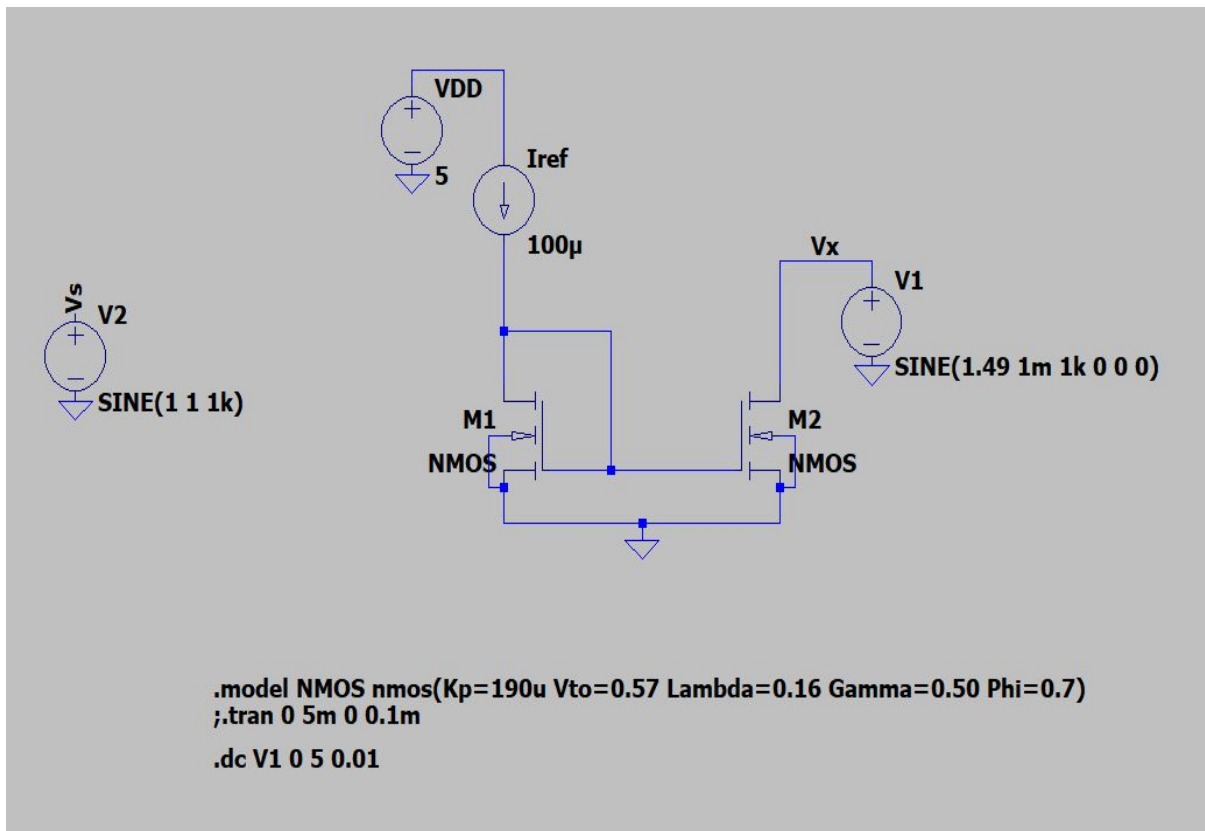

- For cascode current source

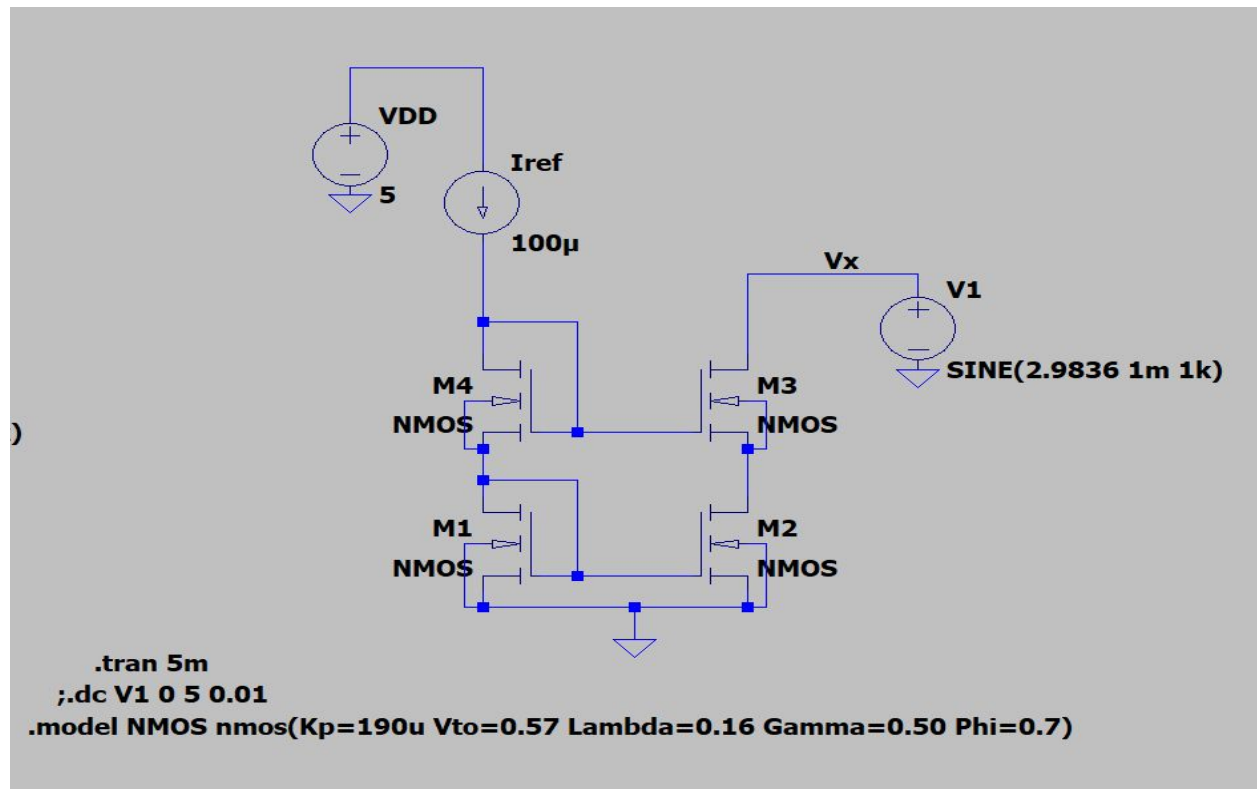

- For low voltage cascode current source

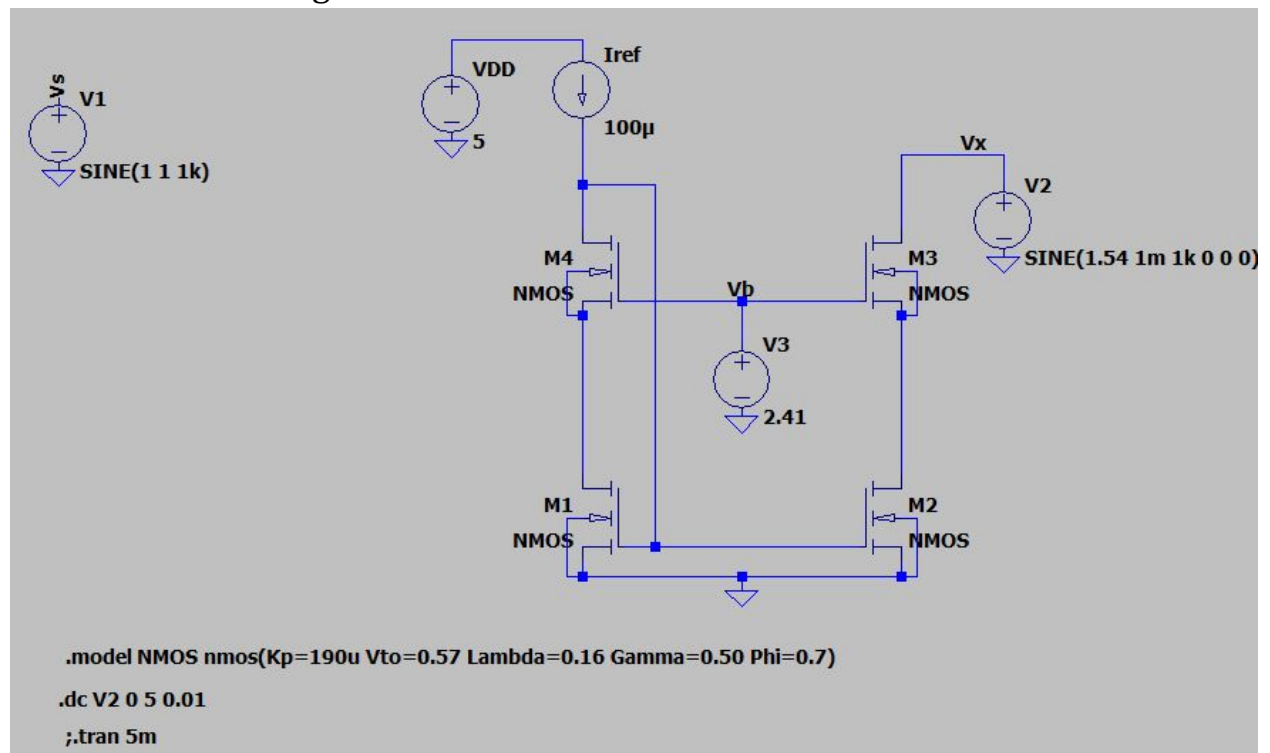


Procedure:


- To design a basic current source of 100uA, a reference current source was applied to M1(see schematic diagram). Further, a mirror ckt was made.
- Then, DC sweep of voltage source V1 was done and I_x was plotted to determine minimum voltage required across the current source to replicate the reference current at output node.
- Now, we applied an external voltage (1mV sinusoid with DC offset equal to the required minimum voltage) and measured peak to peak current at the output node to determine output impedance. ($R_o = \Delta V_x / \Delta I_x$)
- Similar process was done for cascode and low voltage cascode current source.

Waveforms:

Basic Current Source:

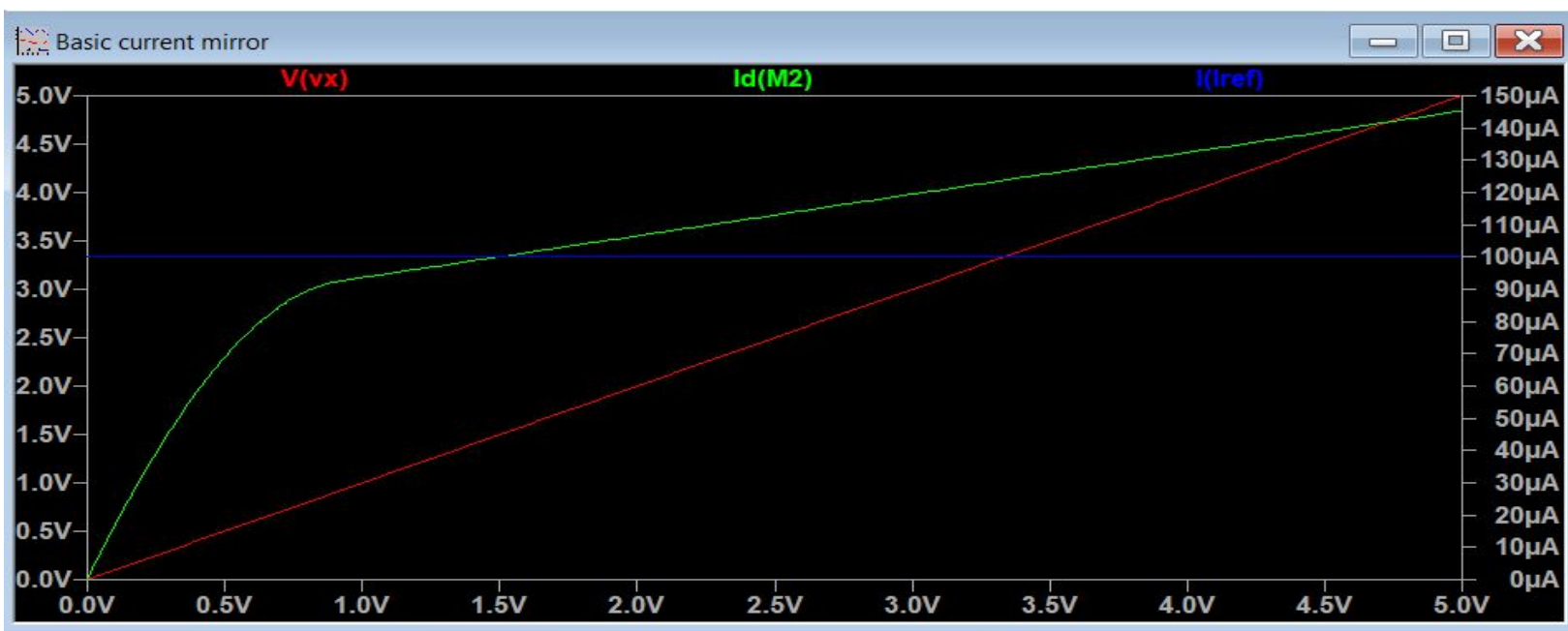


M2(I_d vs V_x)

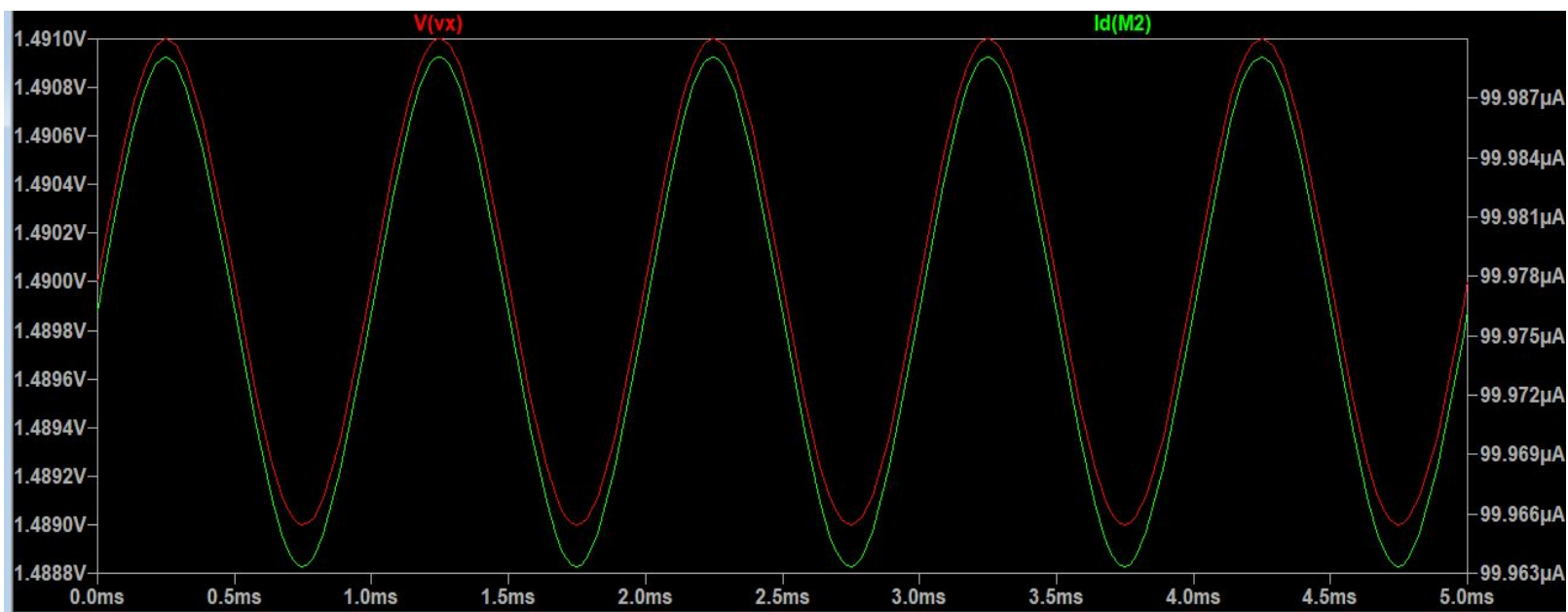


Curve for R_o

Cascode current source:

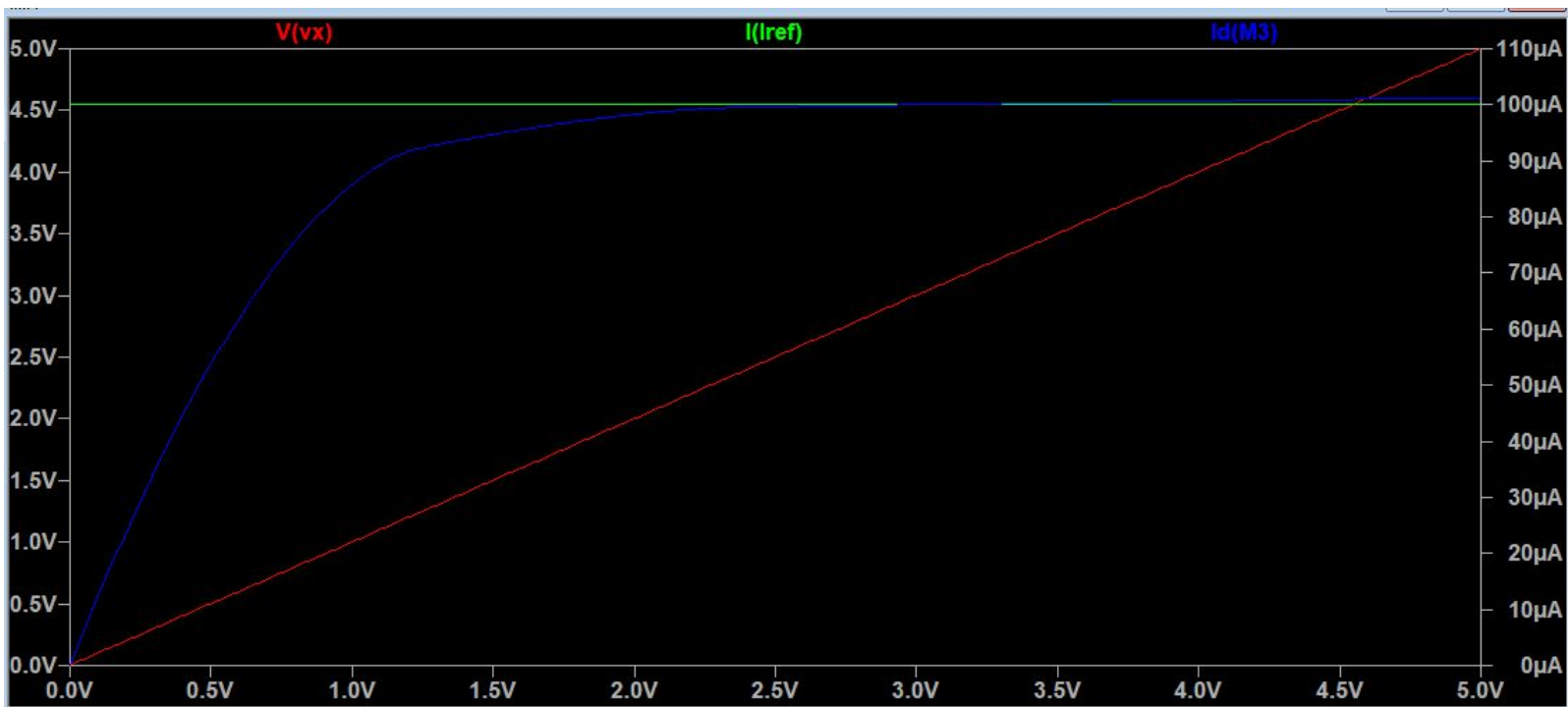


$M3(I_d \text{ vs } V_x)$

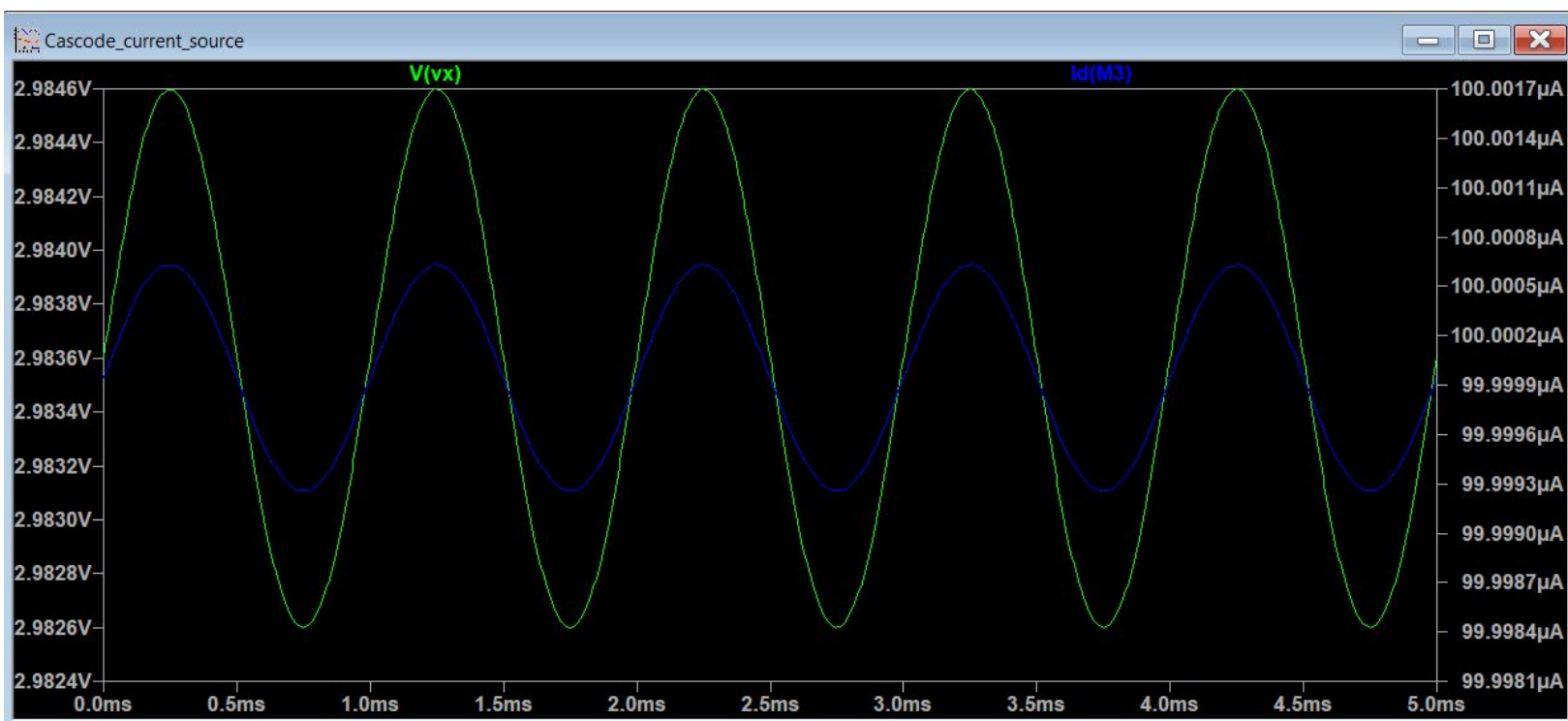


Curve for R_o

Low Voltage Cascode current source:

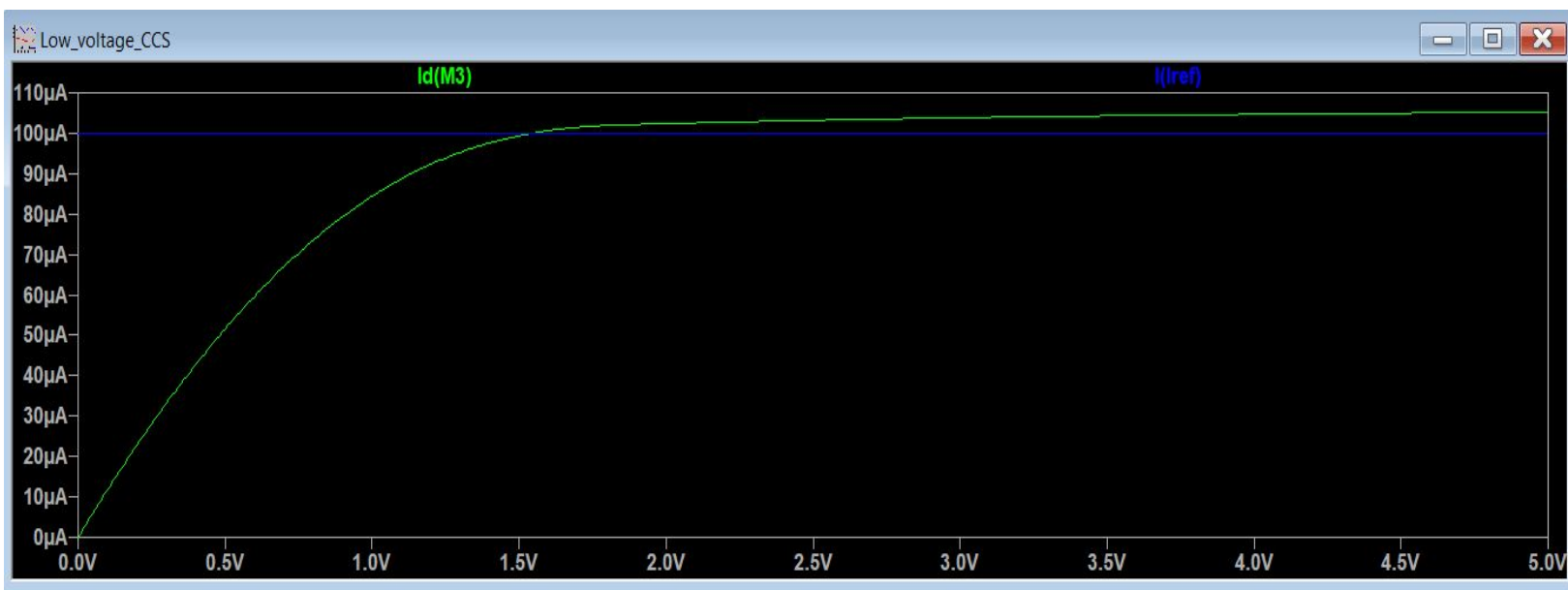

$M3(I_d \text{ vs } V_x)$

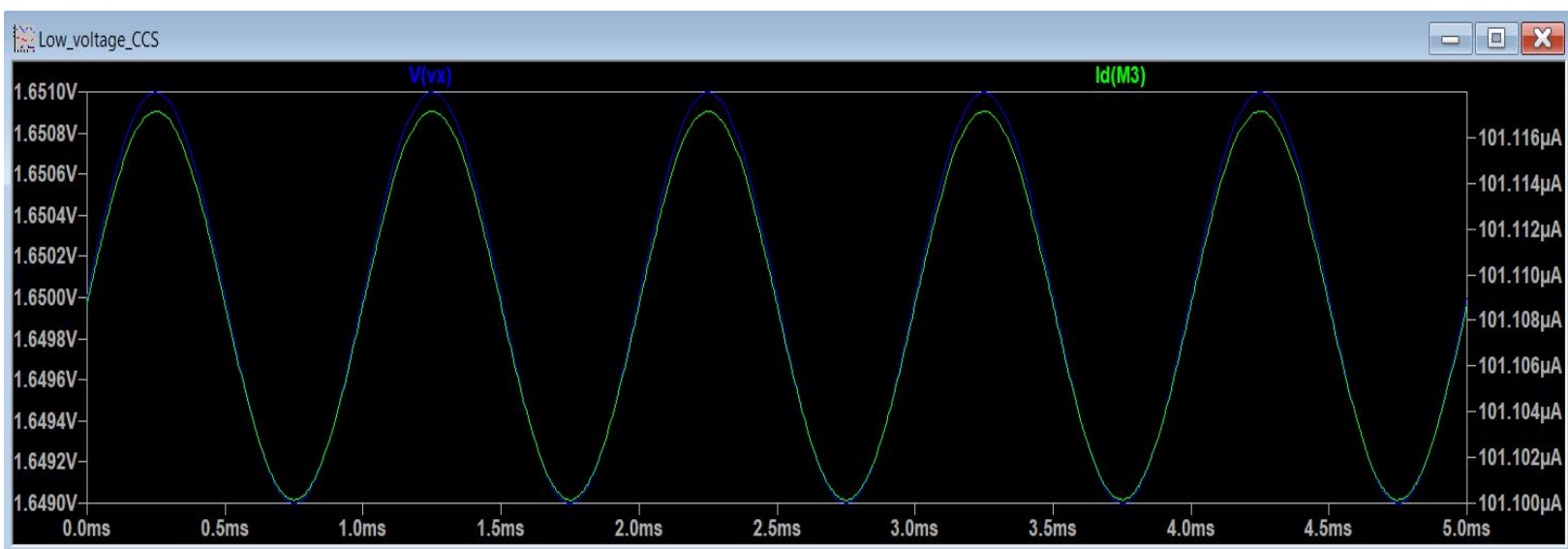

Curve for R_o

Observation Table:

Type	Minimum voltage required(in Volts)	ΔV (in Volts)	ΔI (in nA)	R_o (in $k\Omega$)
Basic current mirror	1.489	0.002	25.8143	77.47
Cascode	2.9836	0.002	1.37477	1453.57
Low voltage Cascode	1.54	0.002	25.9565	77.058

a) Basic current source

$$I_D = \frac{1}{2} K_n' \left(\frac{W}{L} \right) (V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$$

$$I_{DQ1} = \frac{1}{2} (190 \mu) (1) (V_{GS} - 0.57)^2 (1 + 0.016 V_{GS})$$

Or solving this,

$$\boxed{V_{GS} = 1.49 \text{ V}}$$

$$\Rightarrow \text{For } V_i \geq V_{GS} - V_{th}$$

$$V_i \geq 1.49 - 0.57$$

$$\boxed{V_i \geq 0.92} \text{ For } M_2 \text{ to be in saturation.}$$

Calculation of r_o .

$$R_{out} = r_{o2} = \frac{1}{\lambda I_D}$$

$$\text{So, } I_D = \frac{1}{2} K_n' \left(\frac{W}{L} \right) (V_{GS} - 0.57)^2 \Rightarrow I_D = 80.408 \mu\text{A}$$


$$\Rightarrow \boxed{r_{o2} = 77.75 \text{ k}\Omega}$$

b) Cascode current source:

$$R_{out} = [1 + g_{m3} r_{o3}] r_{o2} + r_{o3}$$

$$= \left[1 + \frac{2 I_{D3}}{V_{GS} - V_{th}} \cdot \frac{1}{\lambda I_{D3}} \right] \frac{1}{\lambda I_{D2}} + \frac{1}{\lambda I_{D3}}$$

$$= 1211.55 \text{ k}\Omega$$

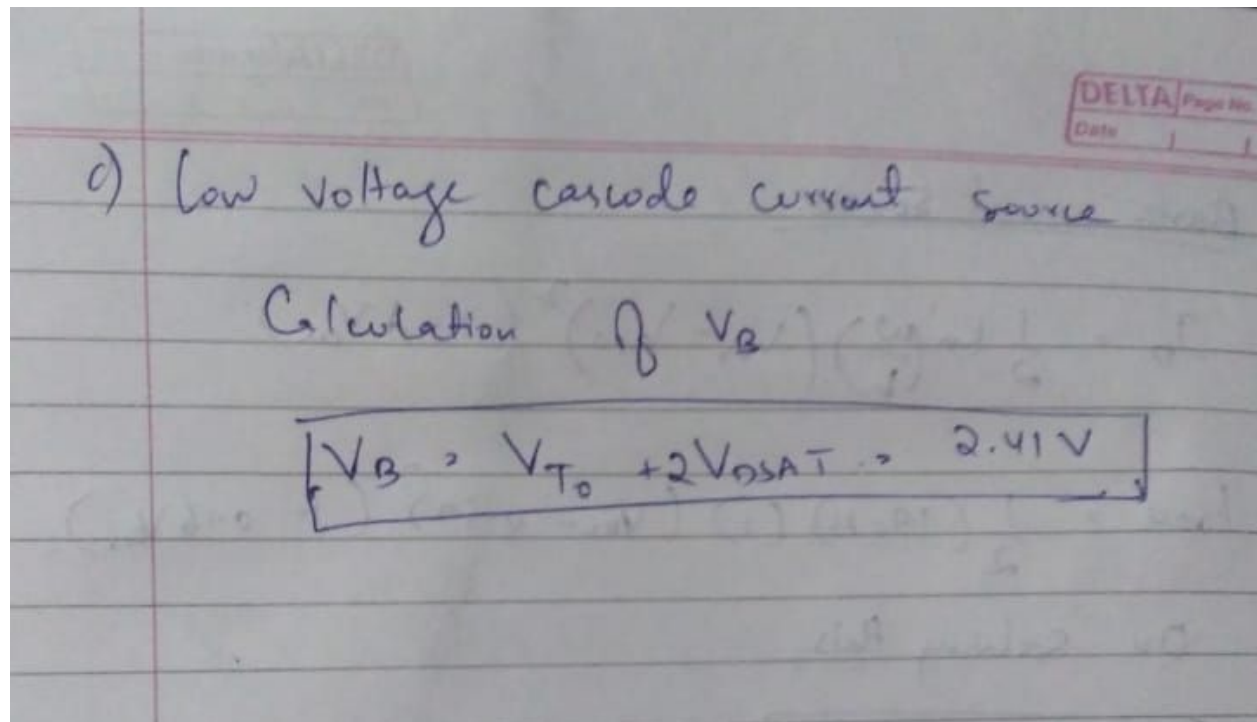

Comparison:

Basic Current mirror:

Advantages:

- Low input Voltage to basic current mirror
- low input impedance makes the input current insensitive to the output impedance of the input source
- high output impedance makes the output current insensitive to the impedance of the output load

Disadvantages:

- 1) The mirror adds noise. This gets worse if there are no emitter resistors. With big enough emitter resistors, the noise can be reduced to an insignificant level.
- 2) Channel length modulation error is high.

Cascode current mirror:

Advantages:

- Higher Output resistance results in less error.
- Channel length modulation error gets cancelled.
- Higher minimum output voltage

Low voltage Cascode :

Advantage:

- This configuration makes it possible to use a higher effective gate-source voltage for the mirror transistors, hence reducing the effect of threshold voltage mismatch on the current mirror gain.
- This configuration has the advantage of simplicity combined with a complete elimination of the need for fixed bias voltages or bias currents in the current mirror.

Disadvantage: it requires a higher input voltage to the current mirror.

Results:

- Assumption :
All mosfet model \Rightarrow **.model NMOS nmos(Kp=190u Vto=0.57
Lambda=0.16 Gamma=0.50 Phi=0.7)**
- In case of Low Voltage Cascode, minimum voltage required is less than the normal cascode.
- Output Resistance in all the cases are very large.